
Datapath Design


Adapted from Mary Jane Irwin

at Penn State University for

Computer Organization and Design, Patterson & Hennessy, © 2005

Clocking Methodologies

 
- ❑ The clocking methodology defines when signals can be read and when they are written
 - An edge-triggered methodology
- ❑ Typical execution
 - read contents of state elements
 - send values through combinational logic
 - write results to one or more state elements



- ❑ Assumes state elements are written on every clock cycle; if not, need explicit write control signal
 - write occurs only when **both** the write control is asserted and the clock edge occurs

Fetching Instructions

 
- ❑ Fetching instructions involves
 - reading the instruction from the Instruction Memory
 - updating the PC to hold the address of the next instruction



- PC is updated every cycle, so it does not need an explicit write control signal
- Instruction Memory is read every cycle, so it doesn't need an explicit read control signal

Decoding Instructions

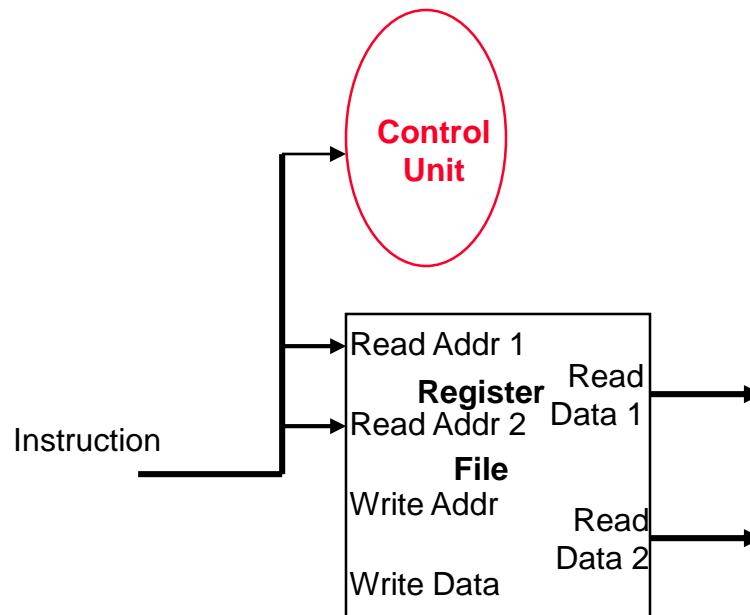
- ❑ Decoding instructions involves
 - sending the fetched instruction's opcode and function field bits to the control unit




- reading two values from the Register File
 - Register File addresses are contained in the instruction

Executing R Format Operations

 - ❑ R format operations (**add**, **sub**, **slt**, **and**, **or**)



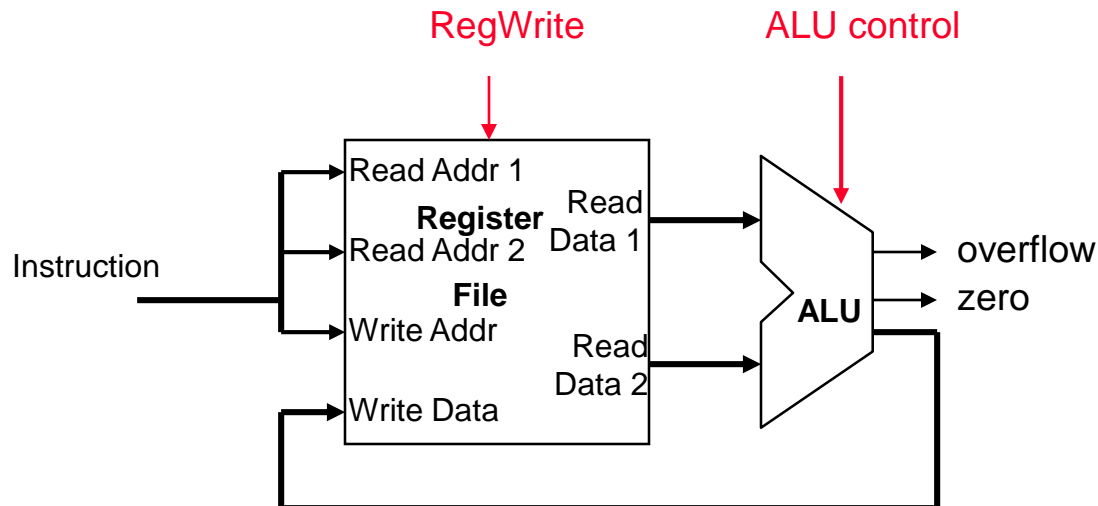
- perform the (**op** and **funct**) operation on values in **rs** and **rt**
- store the result back into the Register File (into location **rd**)



- The Register File is not written every cycle (e.g. **sw**), so we need an explicit write control signal for the Register File

Executing Load and Store Operations

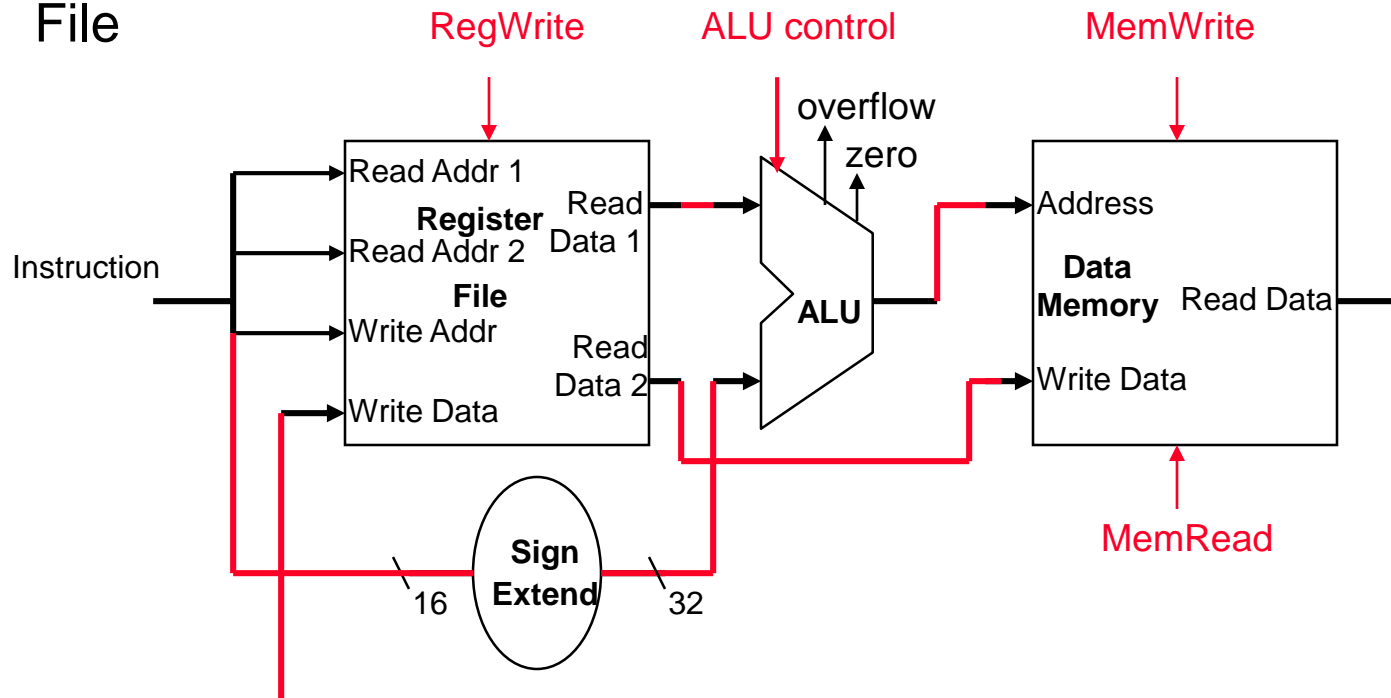
- ❑ Load and store operations involves
 - compute memory address by adding the base register (read from the Register File during decode) to the 16-bit signed-extended offset field in the instruction
 - **store** value (read from the Register File during decode) written to the Data Memory
 - **load** value, read from the Data Memory, written to the Register File



Executing Branch Operations

❑ Branch operations involves

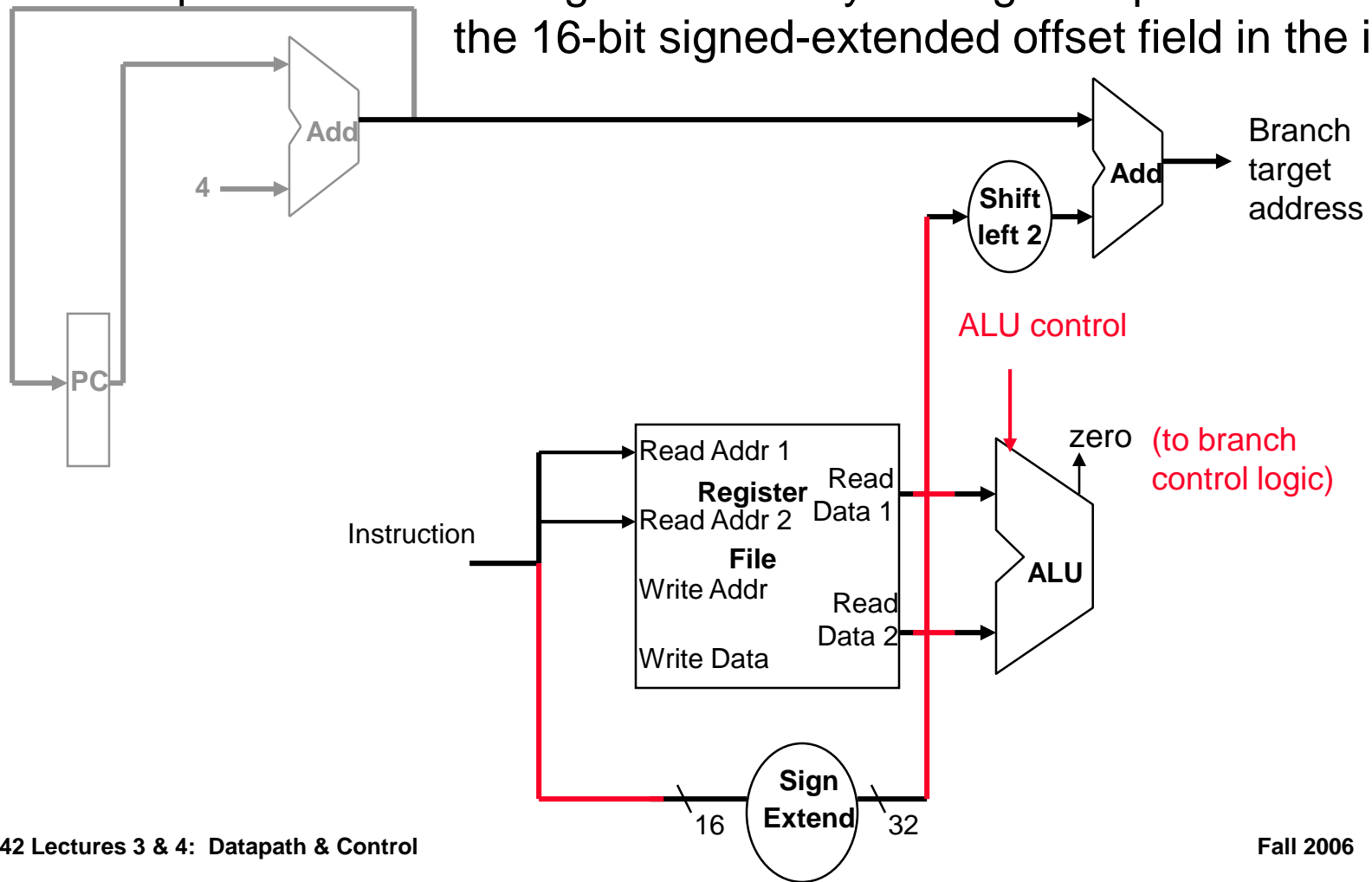
- compare the operands read from the Register File during decode for equality (**zero** ALU output)
- compute the branch target address by adding the updated PC to the 16-bit signed-extended offset field in the instr



Executing Jump Operations

❑ Jump operation involves

 
- replace the lower 28 bits of the PC with the lower 26 bits of the fetched instruction shifted left by 2 bits



Creating a Single Datapath from the Parts

- ❑ Assemble the datapath segments and add control lines and multiplexors as needed
- ❑ **Single cycle** design – fetch, decode and execute each instructions in **one** clock cycle
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
 - **multiplexors** needed at the input of shared elements with control lines to do the selection
 - write signals to control writing to the Register File and Data Memory
- ❑ Cycle time is determined by length of the longest path

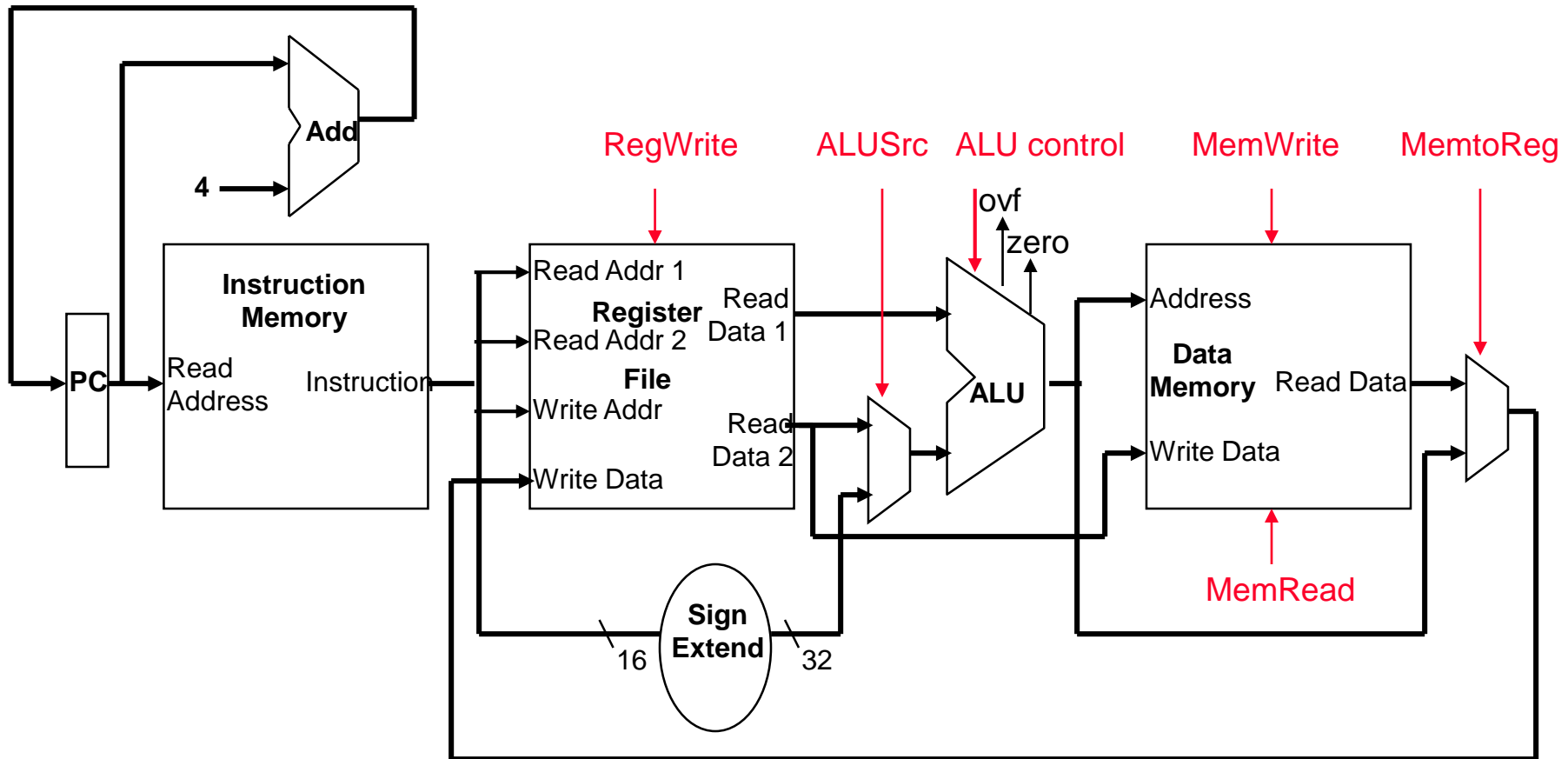
Control signals for Fetch, Reg, and Memory



What determines the values needed on these control signals?


Adding the Control

 - ❑ Selecting the operations to perform (ALU, Register File and Memory read/write)
- ❑ Controlling the flow of data (multiplexor inputs)



❑ Observations


- op field **always** in bits 31-26

 


- addr of registers to be read are **always** specified by the rs field (bits 25-21) and rt field (bits 20-16); for lw and sw rs is the base register
- addr. of register to be written is in one of **two** places – in rt (bits 20-16) for lw; in rd (bits 15-11) for R-type instructions
- offset for beq, lw, and sw **always** in bits 15-0




Single Cycle Datapath with Control Unit

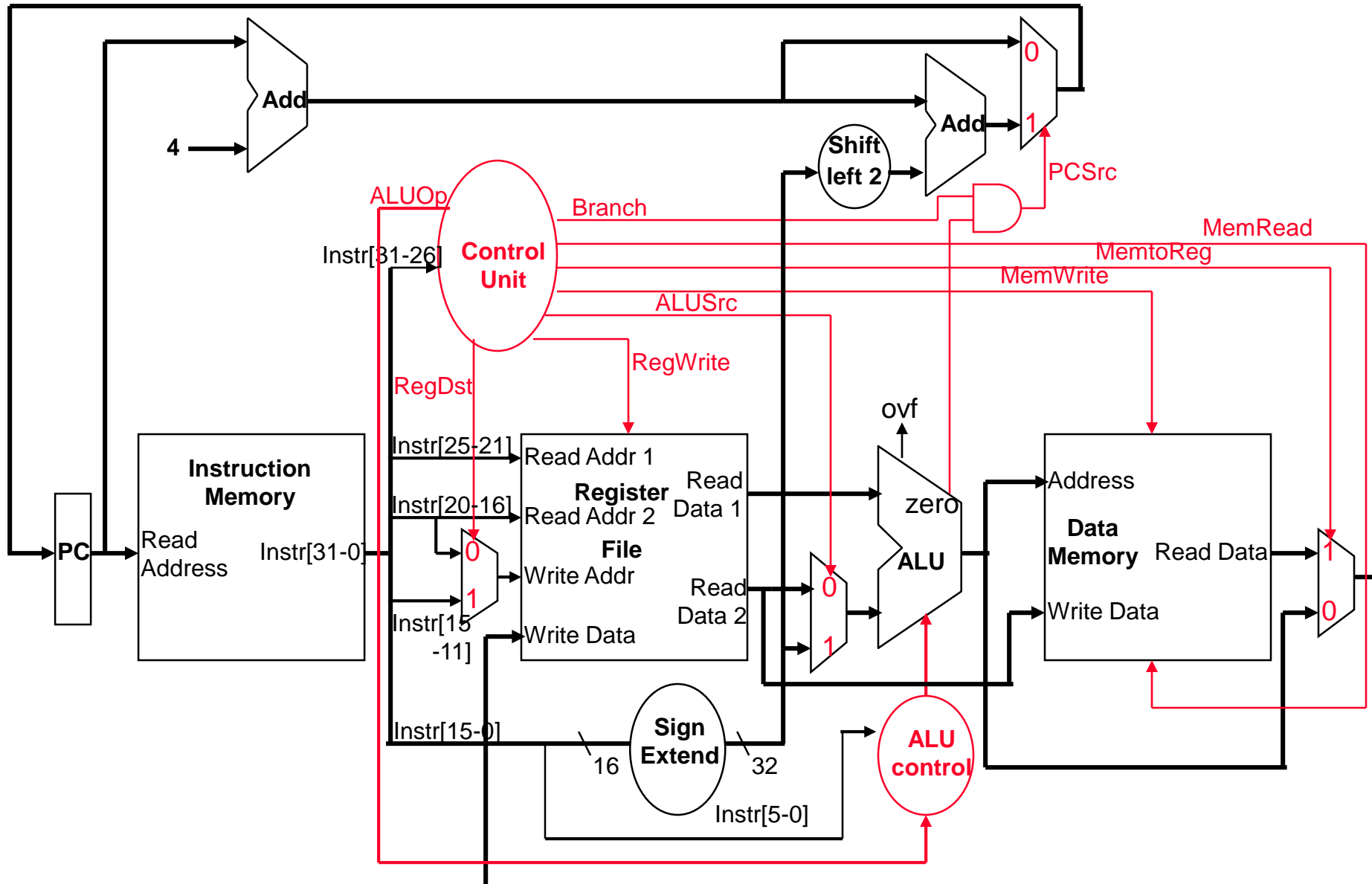


R-type Instruction Data/Control Flow

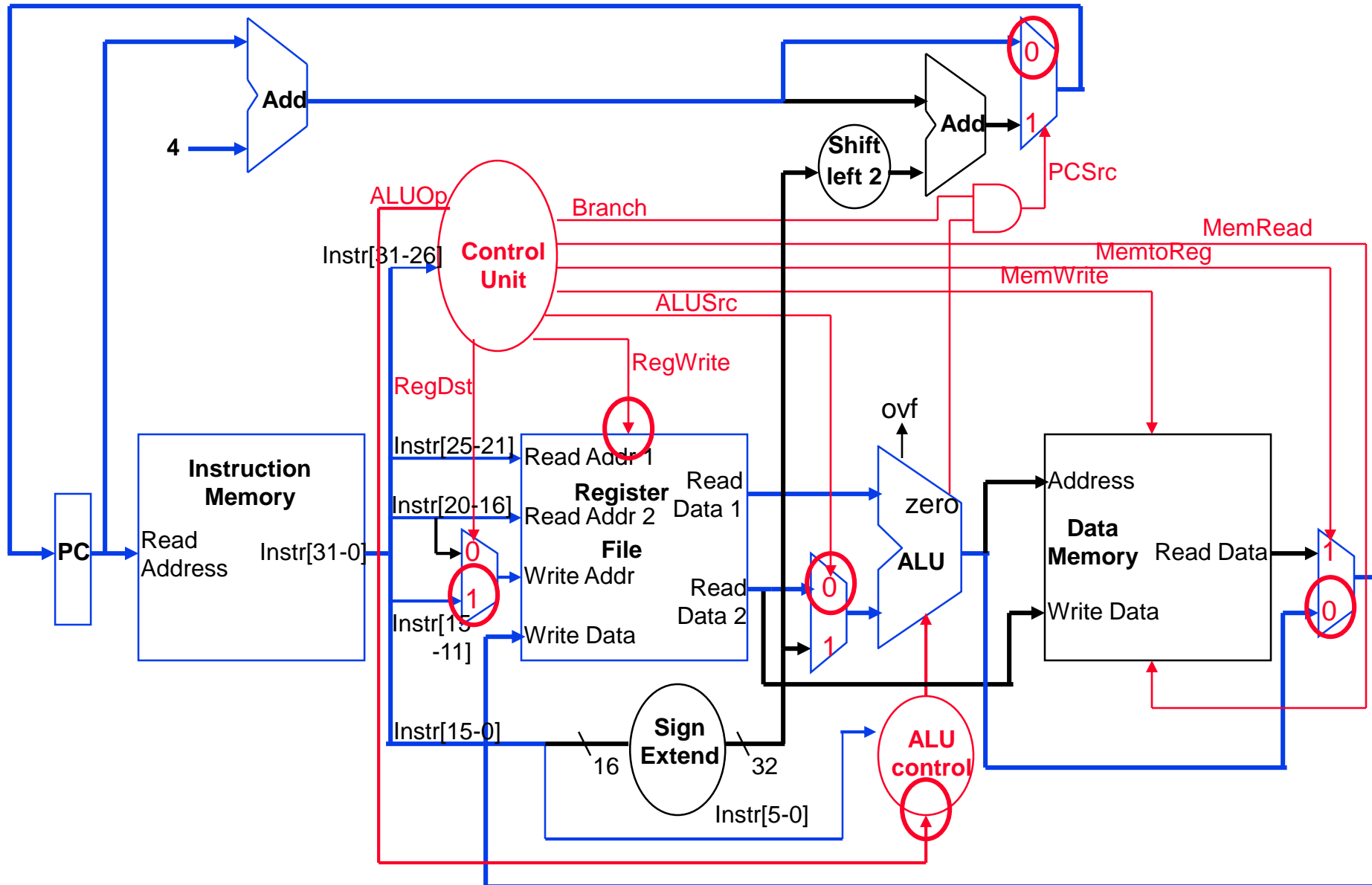


Load Word Instruction Data/Control Flow

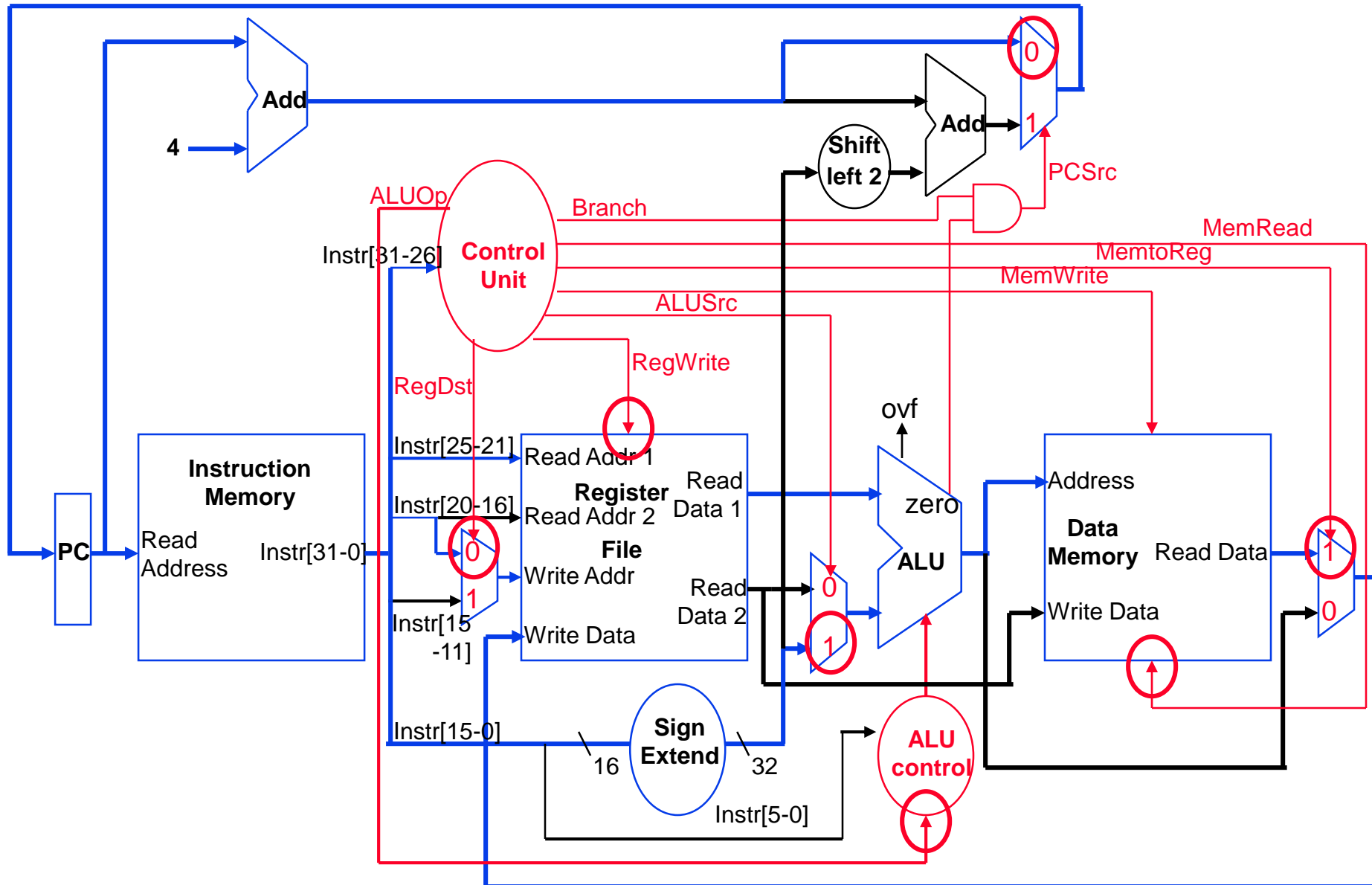

Branch Instruction Data/Control Flow

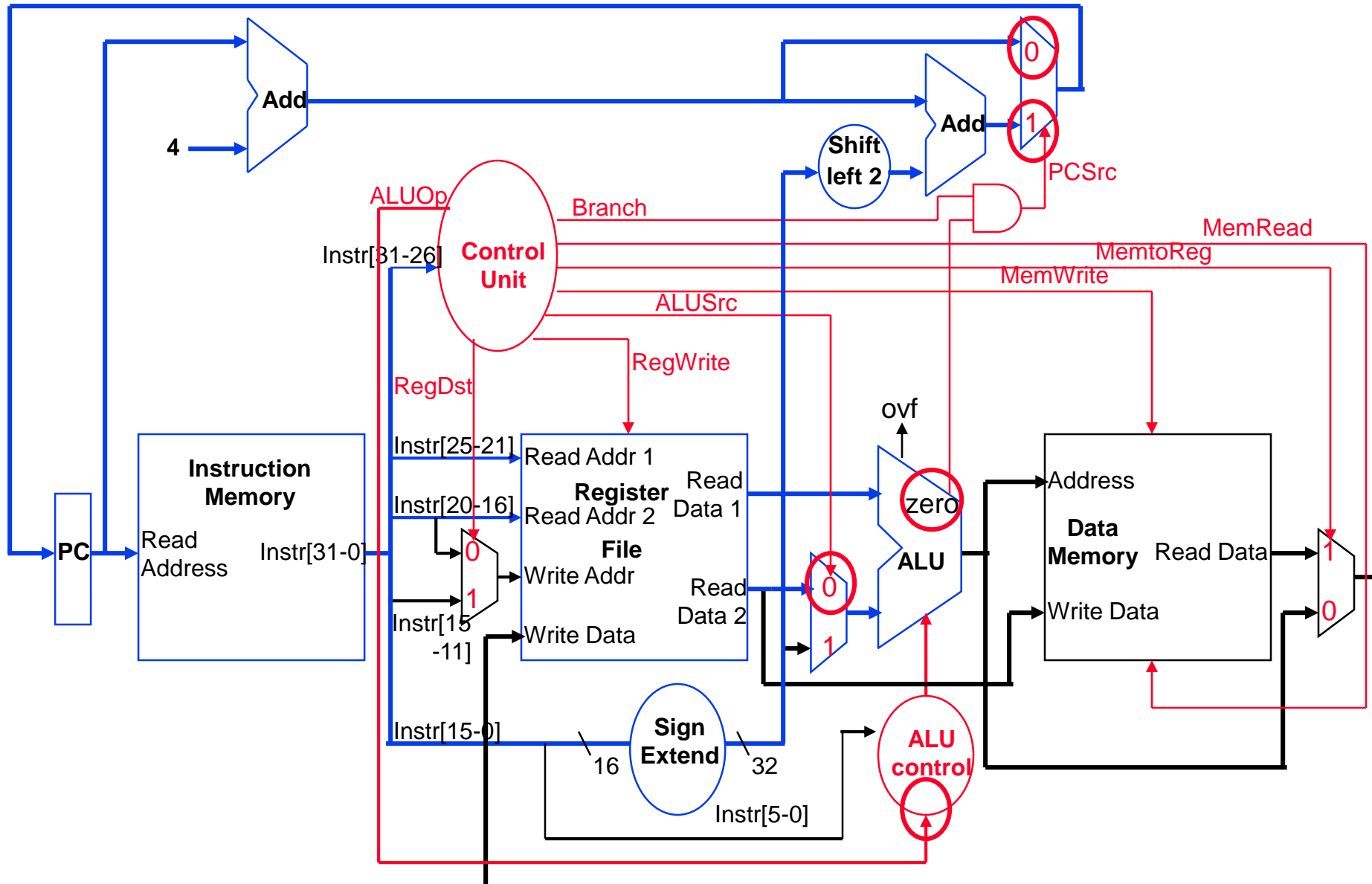


Adding the Jump Operation

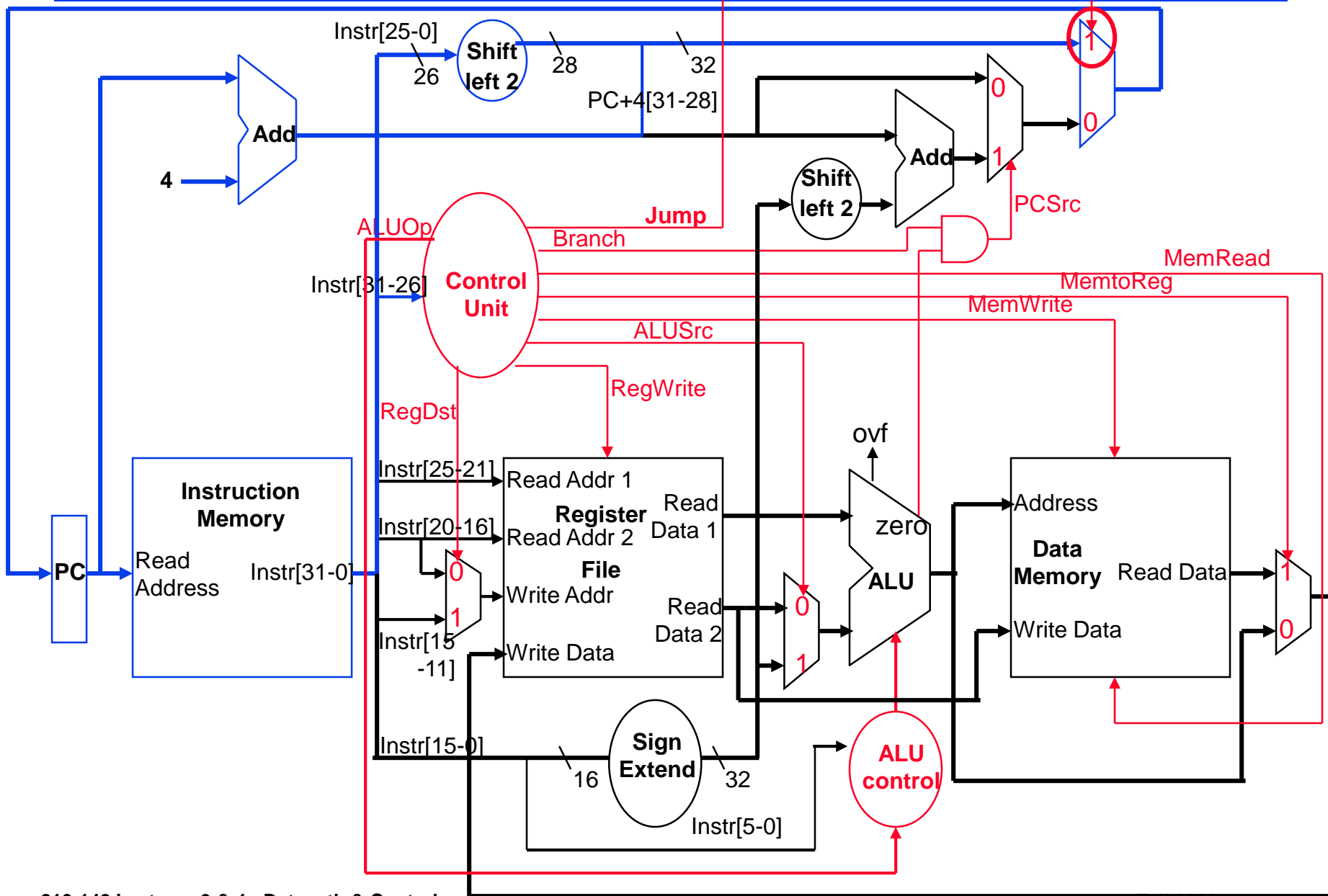

Single Cycle Disadvantages & Advantages

 - ❑ Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the **slowest** instruction
 - especially problematic for more complex instructions like floating point multiply



- ❑ May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle

but

- ❑ Is simple and easy to understand

Multicycle Datapath Approach


- ❑ Let an instruction take more than 1 clock cycle to complete
 - Break up instructions into steps where each *step* takes a cycle while trying to
 - balance the amount of work to be done in each step
 - restrict each cycle to use only one major functional unit
 - Not every instruction takes the *same* number of clock cycles

- ❑ In addition to *faster* clock rates, multicycle allows functional units that can be used more than once per instruction as long as they are used on *different* clock cycles, as a result
 - only need one memory – but only one memory access per cycle
 - need only one ALU/adder – but only one ALU operation per cycle

Multicycle Datapath Approach, con't

❑ At the end of a cycle

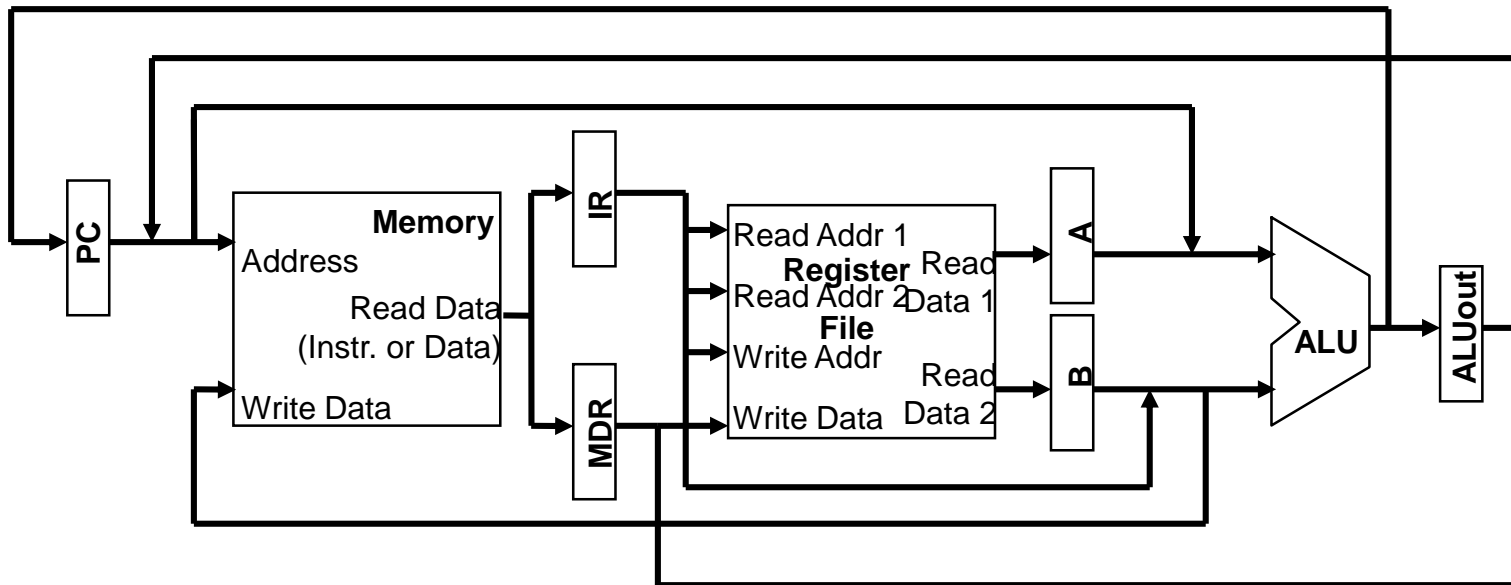- Store values needed in a later cycle by the **current** instruction in an internal register (not visible to the programmer). All (except IR) hold data only between a pair of adjacent clock cycles (no write control signal needed)



IR – Instruction Register


MDR – Memory Data Register

A, B – regfile read data registers

ALUout – ALU output register


- Data used by **subsequent** instructions are stored in programmer visible registers (i.e., register file, PC, or memory)

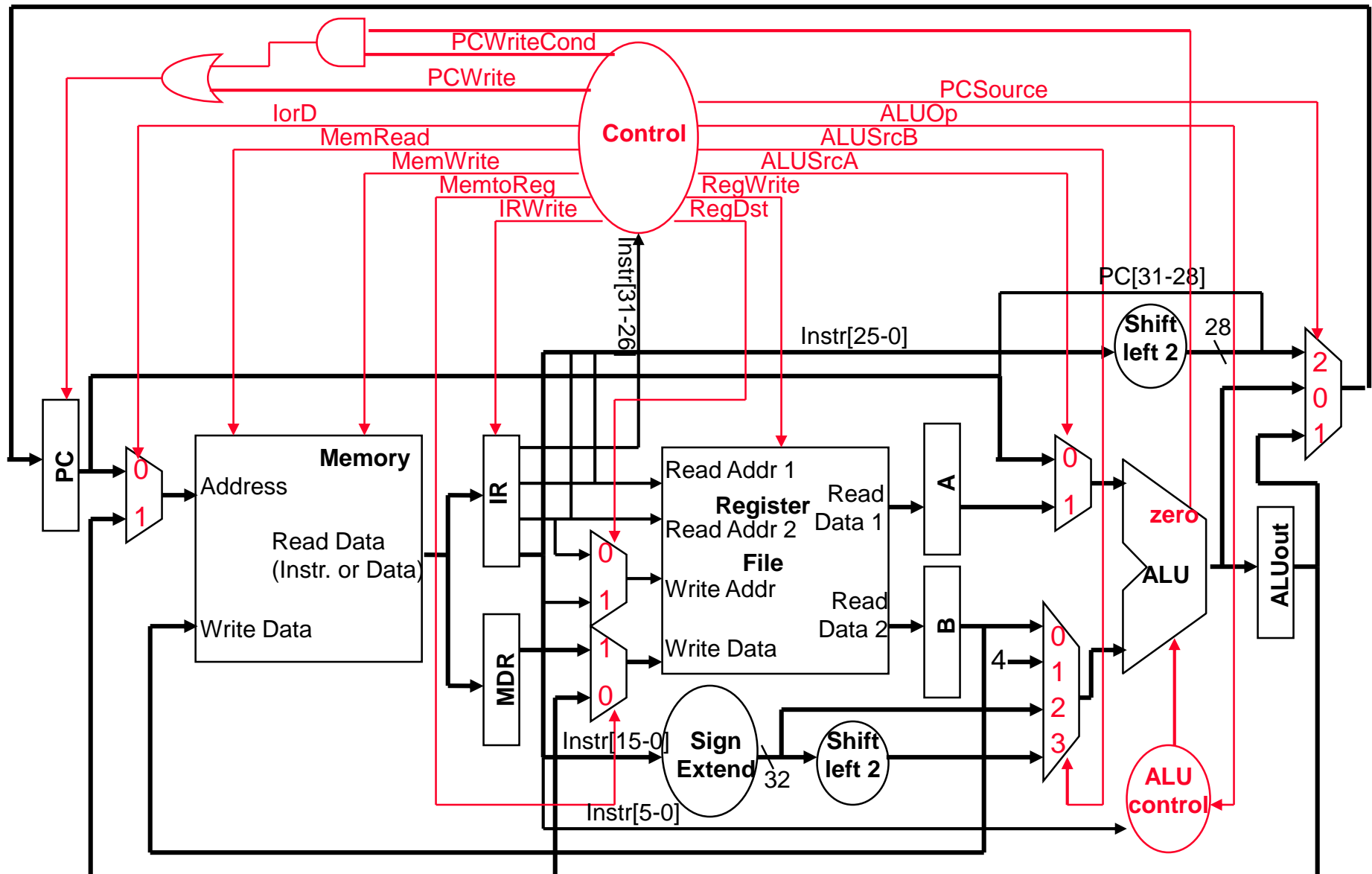The Multicycle Datapath with Control Signals




Multicycle Control Unit

- ❑ Multicycle datapath control signals are not determined solely by the bits in the instruction
 - e.g., op code bits tell what operation the ALU should be doing, but *not* what instruction cycle is to be done next
- ❑ Must use a finite state machine (FSM) for control
 - a set of states (current state stored in State Register)
 - next state function (determined by current state and the input)
 - output function (determined by current state and the input)

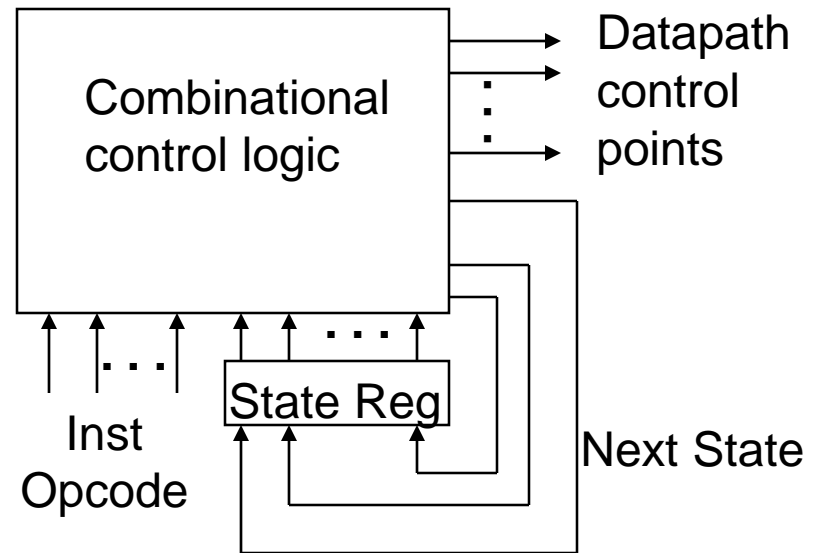

The Five Steps of the Load Instruction

 


- ❑ IFetch: Instruction Fetch and Update PC
- ❑ Dec: Instruction Decode, Register Read, Sign Extend Offset
- ❑ Exec: Execute R-type; Calculate Memory Address; Branch Comparison; Branch and Jump Completion
- ❑ Mem: Memory Read; Memory Write Completion; R-type Completion (RegFile write)
- ❑ WB: Memory Read Completion (RegFile write)

INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!

Multicycle Advantages & Disadvantages

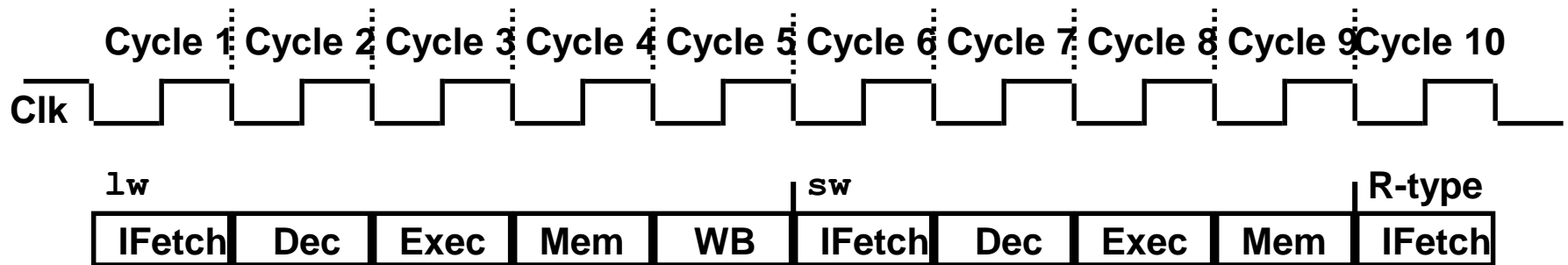- ❑ Uses the clock cycle efficiently – the clock cycle is timed to accommodate the slowest instruction **step**




- ❑ Multicycle implementations allow functional units to be used more than once per instruction as long as they are used on different clock cycles

but

- ❑ Requires additional internal state registers, more muxes, and more complicated (FSM) control

Single Cycle vs. Multiple Cycle Timing

Single Cycle Implementation:

 

Multiple Cycle Implementation:

